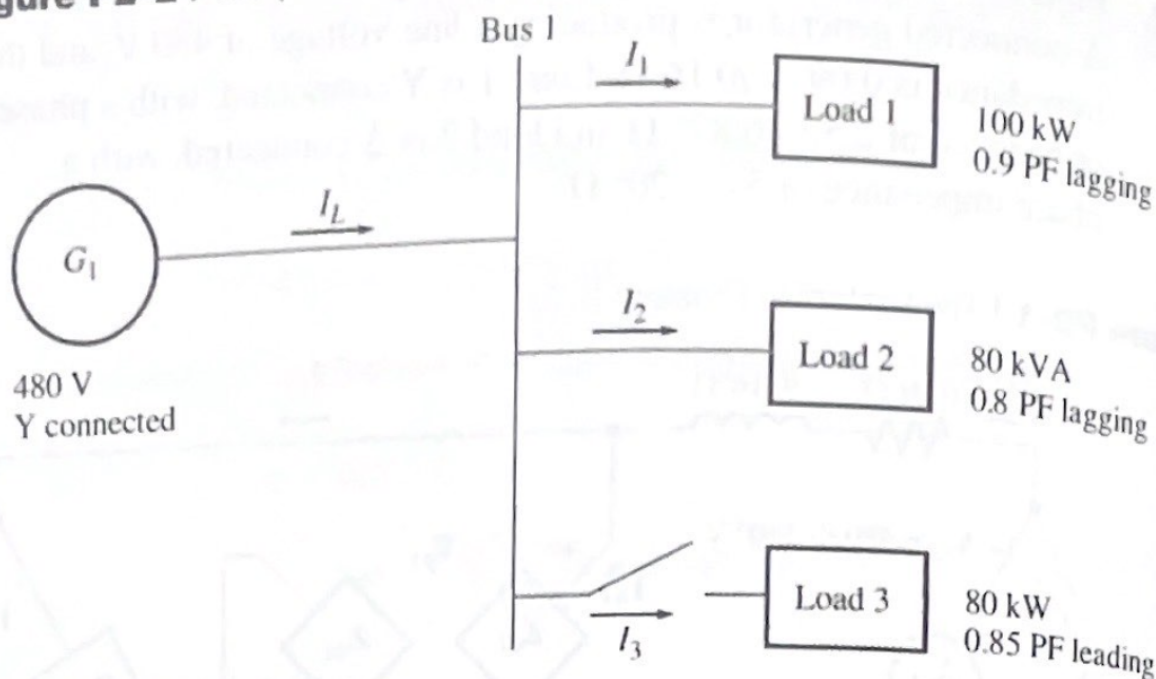


2-3. Figure P2-2 shows a one-line diagram of a simple power system containing a single 480-V generator and three loads. Assume that the transmission lines in this power system are lossless, and answer the following questions.

- Assume that Load 1 is Y connected. What are the phase voltage and currents in that load?
- Assume that Load 2 is Δ connected. What are the phase voltage and currents in that load?
- What real, reactive, and apparent power does the generator supply when the switch is open?
- What is the total line current I_L when the switch is open?
- What real, reactive, and apparent power does the generator supply when the switch is closed?


Figure P2-2 | The power system in Problem 2-3.



- What is the total line current I_L when the switch is closed?
- How does the total line current I_L compare to the sum of the three individual currents $I_1 + I_2 + I_3$? If they are not equal, why not?

- 2-6.** Figure P2-4 shows a one-line diagram of a small 480-V distribution system in an industrial plant. An engineer working at the plant wishes to calculate the current that will be drawn from the power utility company with and without the capacitor bank switched into the system. For the purposes of this calculation, the engineer will assume that the lines in the system have zero impedance.

Figure P2-4 | The system in Problem 2-6.

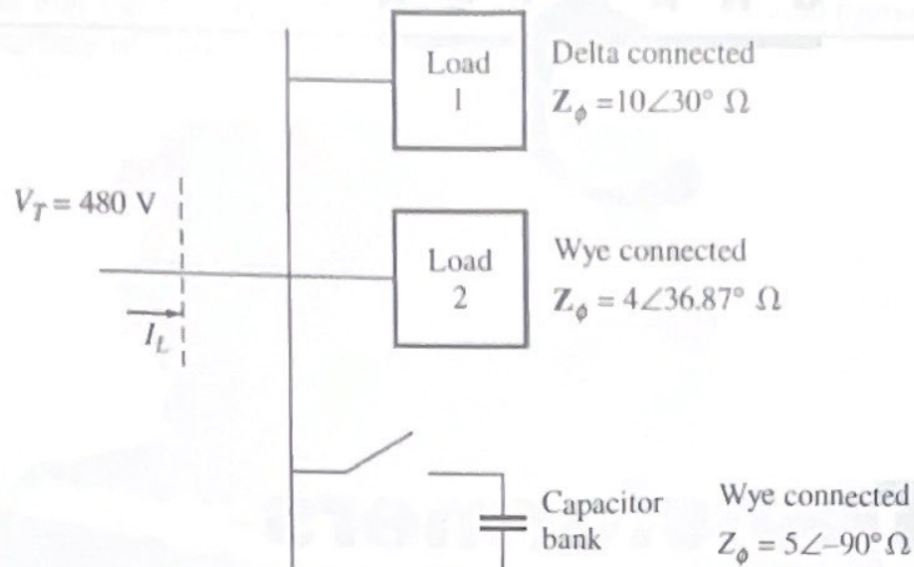

- If the switch shown is open, find the real, reactive, and apparent powers in the system. Find the total current supplied to the distribution system by the utility.
- Repeat part (a) with the switch closed.
- What happened to the total current supplied by the power system when the switch closed? Why?