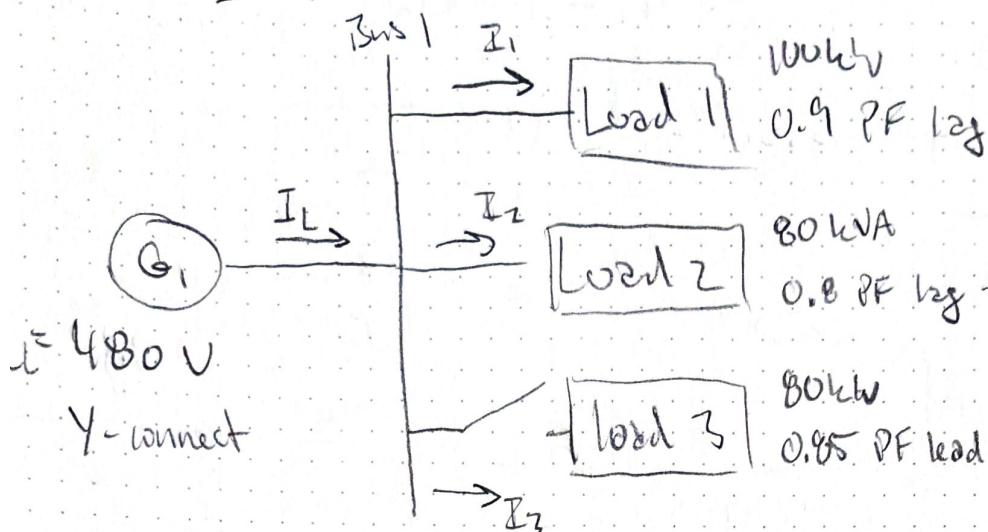


EE347 HW 1

Text 2-3



2) Load 1 Y-connect, what are phase voltages and currents in load?

$$V_{\phi_1} = \frac{480\text{V}}{\sqrt{3}} = 277\text{V}$$

$$P = 3V_{\phi} I_{\phi} \cos\theta$$

$$I_{\phi_1} = \frac{P}{3V_{\phi_1} \cos\theta} = \frac{100\text{kW}}{3(277\text{V})0.9} = 133.7 \text{ A}$$

3) Load 2 Δ-connect, find voltage & current

$$V_{\phi_2} = V_{ll} = 480\text{V}$$

$$I_{\phi_2} = \frac{S}{3V_{\phi_2}} = \frac{80\text{kVA}}{3(480\text{V})} = 55.6 \text{ A}$$

$$c) P_G = P_1 + P_2 \quad Q_G = Q_1 + Q_2 \quad S_G = \sqrt{P_G^2 + Q_G^2}$$

$$P_1 = 100\text{kW}$$

$$Q_1 = (100\text{kW}) \tan(\cos^{-1}(0.9))$$

$$= 48.4 \text{kVA}_r$$


$$P_2 = (80\text{kVA})(0.8)$$

$$Q_2 = (80\text{kVA}) \sin(\cos^{-1}(0.8))$$

$$= 48 \text{kVA}_r$$

$$P_G = 164 \text{ kW}$$

$$Q_G = 96.4 \text{kVA}_r$$

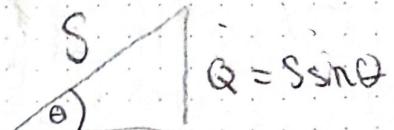

$$P = S \cos\theta$$

$$S = \frac{P}{\cos\theta} = \frac{Q}{\sin\theta}$$

$$Q = P \tan\theta$$

$$P = \frac{Q}{\tan\theta}$$

$$d) P = \sqrt{3} V_{U_L} I_L \cos \Theta \quad \Theta = \tan^{-1} \left(\frac{Q_G}{P_G} \right) = 30,45^\circ$$

$$I_L = \frac{P_G}{\sqrt{3} V_{U_L} \cos \Theta} \quad P = 164 \text{ kW}$$

$$\begin{aligned} &= \frac{164 \text{ kW}}{\sqrt{3}(480 \text{ V})(0,86)} \\ &= 1228,8 \text{ A} \end{aligned}$$

$$e) P_3 = 80 \text{ kW} \quad \text{PF} = 0,85 \text{ lead}$$

$$Q_3 = P_3 \tan(-\cos^{-1}(0,85)) \stackrel{\text{lead}}{=} -49,6 \text{ kVAr} \quad \text{leading}$$

$$P_G = P_1 + P_2 + P_3 = 244 \text{ kW}$$

$$Q_G = Q_1 + Q_2 + Q_3 = 46,8 \text{ kVAr}$$

$$S_G = \sqrt{P_G^2 + Q_G^2} = 248,4 \text{ kVA}$$

$$f) I_L = \frac{P_G}{\sqrt{3} V_{U_L} \cos \Theta} \quad \Theta = \tan^{-1} \left(\frac{Q_G}{P_G} \right) = 10,86^\circ$$

$$\cos \Theta = 0,982$$

$$I_L = \frac{244 \text{ kW}}{\sqrt{3}(480 \text{ V}) \cos(10,86^\circ)}$$

$$= 298,8 \text{ A}$$

2) Compare total I_L to $I_1 + I_2 + I_3$

$$I_L = 298.8 \text{ A}$$

$$I_1 = \frac{P_1}{\sqrt{3} V_{LL} PF_1} = \frac{100 \text{ kW}}{\sqrt{3}(480 \text{ V})(0.9)} = 133.6 \text{ A}$$

$$I_2 = \frac{S_1}{\sqrt{3} V_{LL}} = \frac{80 \text{ kVA}}{\sqrt{3}(480 \text{ V})} = 96.2 \text{ A}$$


$$I_3 = \frac{P_3}{\sqrt{3} V_{LL} PF_3} = \frac{80 \text{ kW}}{\sqrt{3}(480)(0.85)} = 113.2 \text{ A}$$

$$I_1 + I_2 + I_3 = \boxed{343 \text{ A}}$$

is greater than $I_L = 299 \text{ A}$

because each load is drawing current at a different power factor angle, and the 3rd load has a leading current, opposing the other two.

2-6

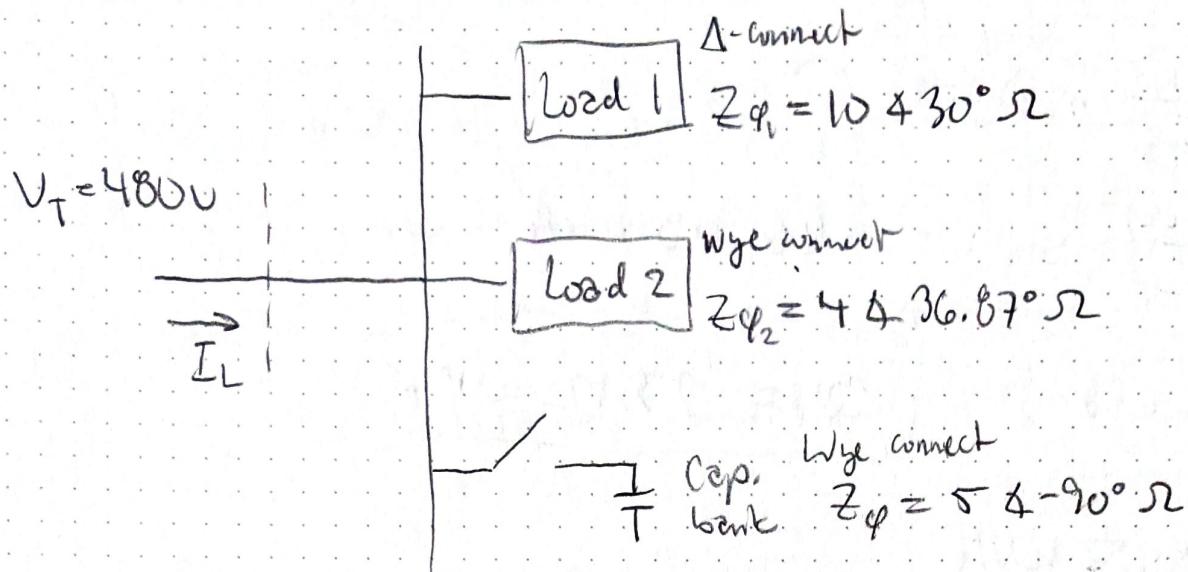

d) open switch

$$P_1 = 3 \frac{V_T^2}{Z_{q_1}} \cos \theta_1 = 3 \left(\frac{480V^2}{10\Omega} \right) \cos(30^\circ) = 59.9 \text{ kW}$$

$$Q_1 = 3 \frac{V_T^2}{Z_{q_1}} \sin \theta_1 = 3 \left(\frac{480V^2}{10\Omega} \right) \sin(30^\circ) = 34.6 \text{ kVAR}$$

$$P_2 = 3 \frac{(V_T/\sqrt{3})^2}{Z_{q_2}} \cos \theta_2 = 46.0 \text{ kW}$$

$$Q_2 = 3 \frac{(V_T/\sqrt{3})^2}{Z_{q_2}} \sin \theta_2 = 34.6 \text{ kVAR}$$

$$P_T = P_1 + P_2 = 106 \text{ kW}$$

$$Q_T = Q_1 + Q_2 = 69.2 \text{ kVAR}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = 126.6 \text{ kVA}$$

$$I_L = \frac{P_T}{\sqrt{3} V_T \text{PF}}$$

$$\text{PF} = \cos(\tan^{-1}\left(\frac{Q_T}{P_T}\right)) = 0.837$$

by

$$= \frac{106 \text{ kW}}{\sqrt{3}(480V)(0.837)}$$

$$= 152.3 \text{ A}$$

b) closed switch

$$P_3 = 3 \frac{(V_t/\sqrt{3})^2}{Z_{Q_3}} \cos\theta = 0$$

$$Q_3 = 3 \frac{(V_t/\sqrt{3})^2}{Z_{Q_3}} \sin\theta = -46.08 \text{ kVA} \text{r}$$

$$P_T = 106 \text{ kW}$$

$$Q_T = 23.12 \text{ kVA} \text{r}$$

$$S_T = 108.5 \text{ kVA}$$

$$\text{PF} = \cos(\tan^{-1}\left(\frac{Q_T}{P_T}\right)) = 0.977$$

$$I_L = \frac{P_T}{\sqrt{3} V_t \text{PF}} = 130.5 \text{ A}$$

c) The total current decreased since the resistance of the system is reduced and there is less reactive power.

Prob. 1

$$\bar{V}_S = 480V \angle 0^\circ$$

- a) 1, 9 kW HID, PF = 1.0
- b) 1, 5 tonne heat pump, COP = 1.75, PF_b = 0.95 lag
- c) 2, 5 HP, n = 90% (lathes), PF_c = 0.79 lag
- d) 3, elec autoclaves, 10kWth/h, n = 98%, PF = 0.97 lag

$$a) \bar{S}_a = 9kW + j0 = \sqrt{3} \bar{V}_S \bar{I}_a^*$$

$$\bar{I}_a = \frac{9kW + j0}{\sqrt{3}(480V \angle 0^\circ)} = 10.8 \angle 0^\circ A$$

$$b) 3.5 \text{ kW / tonne thermal}$$

$$P_{\text{thrm}} = (5 \text{ tonnes})(3.5 \text{ kW/tonne}) = 17.5 \text{ kW thermal}$$

$$P_{\text{elec}} = \frac{P_{\text{thrm}}}{COP} = 10 \text{ kW} = P_b$$

$$\Theta_b = \cos^{-1}(PF_b) = 18.2^\circ \quad S_2 = \frac{P_b}{PF_b} = 10.5 \text{ kVA}$$

$$\bar{S}_b = 10.5 \text{ kVA} \angle 18.2^\circ = \sqrt{3} \bar{V}_S \bar{I}_b^*$$

$$\bar{I}_b = \frac{\bar{S}^*}{\sqrt{3} \bar{V}_S} = \frac{(10.5 \text{ kVA} \angle 18.2^\circ)^*}{\sqrt{3}(480V \angle 0^\circ)}$$

$$= 12.6 \angle 18.2^\circ A$$

$$c) P_{\text{mech}, \text{kW}} = (0.746 \text{ kW/HP}) P_{\text{mech}, \text{HP}} = 3.73 \text{ kW}$$

$$P_{\text{elec}} = \frac{P_{\text{mech}, \text{kW}}}{\eta} = 4.14 \text{ kW}$$

$$P_c = 2 P_{\text{elec}} = 8.3 \text{ kW}$$

$$S_c = \frac{P_c}{\text{PF}_c} = 10.5 \text{ kVA}$$

$$\Theta_c = \cos^{-1}(\text{PF}_c) = 37.8^\circ$$

$$\bar{I}_c = \frac{(10 \text{ kVA} \times 37.8^\circ)}{\sqrt{3} (480 \text{ V} \times 0^\circ)} = 12 \times 37.8 \text{ A}$$

d) 3 antriebe $10 \text{ kW} \cdot \text{BTh}/\text{h}$, $\eta = 98\%$, $\text{PF}_d = 0.97 \text{ lag}$

$$1 \text{ W} / 3.41 \text{ BTh/h} \rightarrow 10 \text{ kW} \cdot \text{BTh}/\text{h} / 3.41 \text{ BTh/h/W} = 2.93 \text{ kW}_{\text{thermal}}$$

$$P_{\text{elec}} = \frac{P_{\text{thermal}}}{\eta} = 2.96 \text{ kW}$$

$$P_d = 3 P_{\text{elec}} = 8.88 \text{ kW} \quad S_d = \frac{P_d}{\text{PF}_d} = 9.15 \text{ kVA}$$

$$\Theta_d = \cos^{-1}(\text{PF}_d) = 14^\circ$$

$$\bar{I}_d = \frac{9.15 \text{ kVA} \times 14^\circ}{\sqrt{3} (480 \text{ V})} = 11 \times 14^\circ \text{ A}$$

Switch lighting system (a) with

• T8 fluorescent 25% less consumption, $P_f = 0.91 \text{ lead}$

$$P_f = 0.75 P_o = (0.75)(9 \text{ kW}) = 6.75 \text{ kW}$$

$$S_f = \frac{P_f}{P_f} = 7.4 \text{ kVA} \quad \theta_f = \cos^{-1}(P_f) = -24.5^\circ \text{ leading}$$

$$\bar{S}_f = 7.4 \text{ kVA } \angle -24.5^\circ$$

$$\bar{I}_f = \frac{\bar{S}_f}{\sqrt{3} V_s} = 8.9 \angle -24.5^\circ \text{ A lead}$$

$$\bar{S}_1 = \bar{S}_a + \bar{S}_b + \bar{S}_c + \bar{S}_d = 38 \angle 18.3^\circ \text{ kVA}$$

$$\bar{S}_2 = \bar{S}_f + \bar{S}_b + \bar{S}_c + \bar{S}_d = 35 \angle 14.6^\circ \text{ kVA}$$

$$I_1 = \frac{\bar{S}_1}{\sqrt{3} V_s} = \frac{38 \text{ kVA}}{\sqrt{3}(480\text{V})} = 45.7 \text{ A}$$

$$I_2 = \frac{\bar{S}_2}{\sqrt{3} V_s} = \frac{35 \text{ kVA}}{\sqrt{3}(480\text{V})} = 42 \text{ A}$$

for 60°C rating w/ 40°C ambient,

CF = 0.82 from Table 310.15(B)(2)(a)


for 40°C ambient, based on 30°C

Using Table 310.15(B)(16):

for 60°C , $(0.82)I_1 = 37 \text{ A} \rightarrow \text{AWG } 8$

$(0.82)I_2 = 34 \text{ A} \rightarrow \text{AWG } 8$

Prob 2

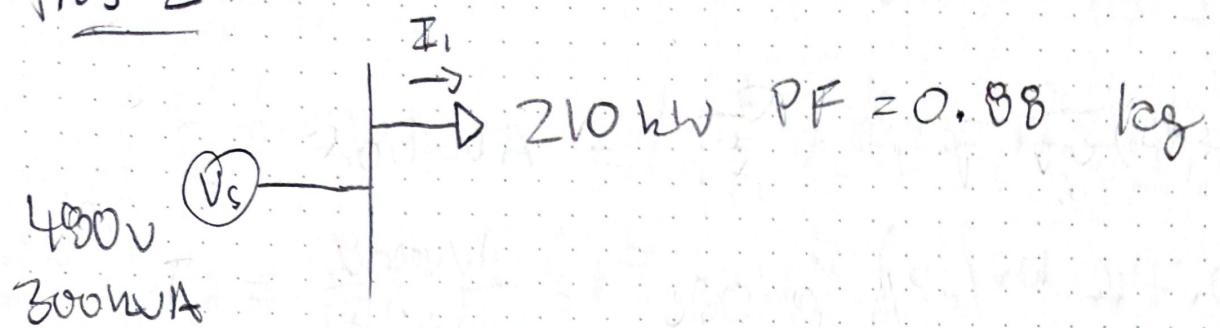

$$S_1 = \frac{P}{PF} = \frac{210 \text{ kW}}{0.88} = 238.6 \text{ kVA}$$

$$I_1 = \frac{S_1}{\sqrt{3} V_s} = \frac{238.6 \text{ kVA}}{\sqrt{3} (480 \text{ V})} = 287 \text{ A}$$

Use CF from Table 310.15(B)(2)(a) for 30°C ambient

temp rating for Al THW = 75°C

ambient temp 36-40°C : CF = 0.88

$$I_1 (0.88) = 253 \text{ A}$$

Use Table 310.15(B)(16) for conductor gauge

Al THW 270 > 253 A

400 kcmil gauge

add two 12 HP lathes ($\eta = 90\%$, $PF = 0.87 \text{ lag}$)

to same branch.

$$P_{\text{mechkw}} = (0.746 \text{ kW/HP}) P_{\text{mechHP}} = 8.95 \text{ kW}$$

$$P_{\text{elec}} = \frac{P_{\text{mechkw}}}{\eta} = 9.95 \text{ kW}$$

$$\rho = 2(P_{\text{elec}}) = 19.9 \text{ kW}$$

$$S = \frac{\rho}{PF} = 22.9 \text{ kVA}$$

$$S_2 = S_1 + S = 261.5 \text{ kVA}$$

$$I_2 = \frac{S_2}{\sqrt{3} V_S} = 314.5 \text{ A}$$

Using the same values from NFPA 70

$$I_2 \text{ CF} = I_2(0.88) = 277 \text{ A}$$

277 A > 270 A max rating for

400 kcmil gauge conductor

FE Prob 1

$S = 2100 \text{ VA}$ w/ $\text{PF} = 0.85$ lagging, $\text{VAr is } \dots$

$$\Theta = \cos^{-1}(\text{PF}) = 31.8^\circ$$


$$Q = S \sin \Theta = 1166.6 \text{ VAr}$$

(A) 1100 VAr since lag $\rightarrow +Q$

FE Prob 2

$$\bar{Z} = 30\Omega + (-j50\Omega) + j90\Omega$$

$$= 30\Omega + j40\Omega$$

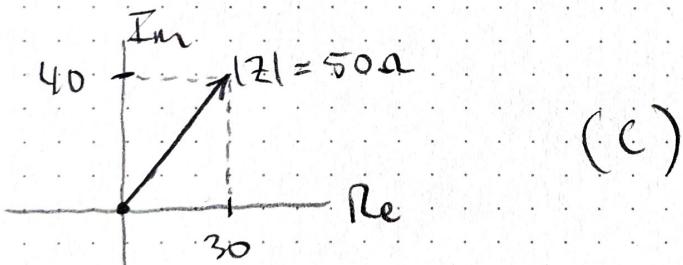

(c)